
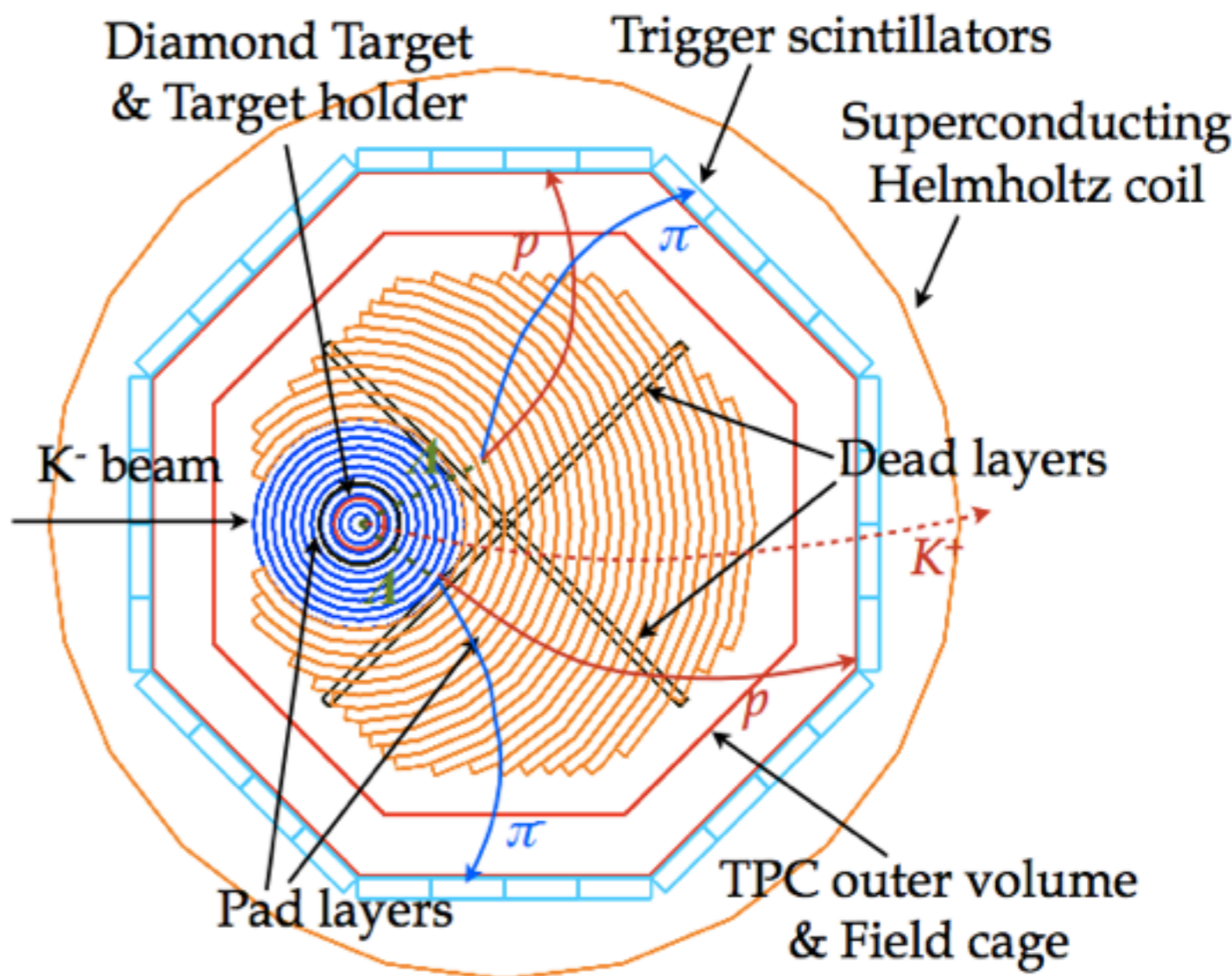


# Development of a MPPC Signal Amplifier Circuit

2016/3/8

Wooseung Jung

# E42 hypTPC

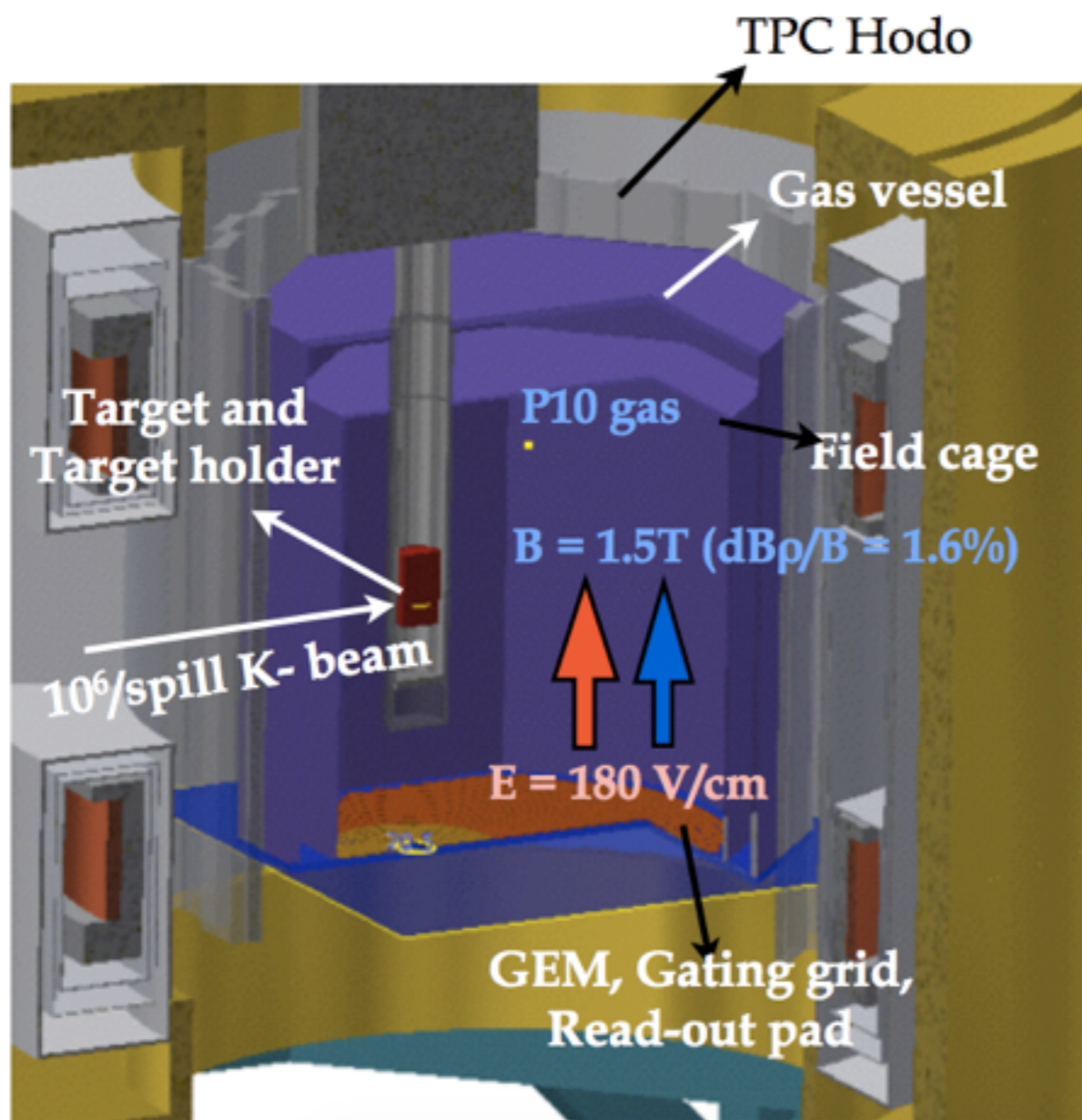



# MPPC?

## MPPC


- multi-pixel photon counter
- photodiode pixels

## Photodiode

- photoelectric effect

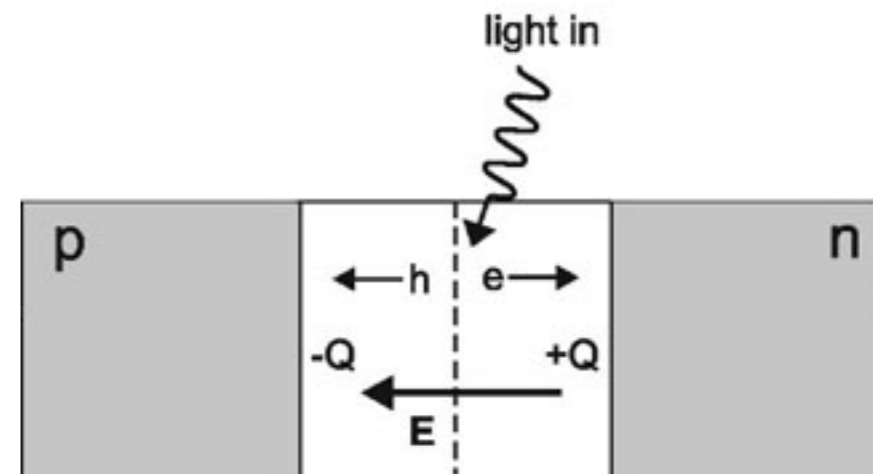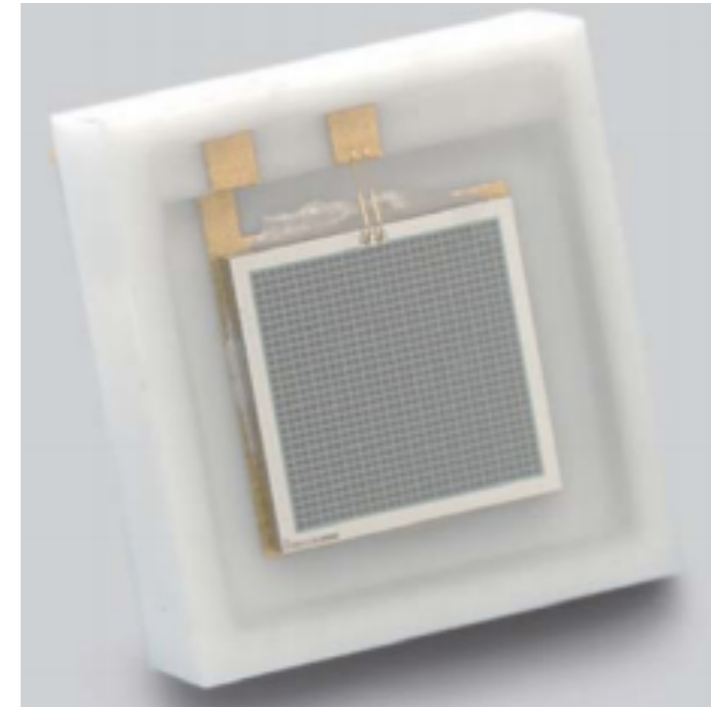



# Si APD

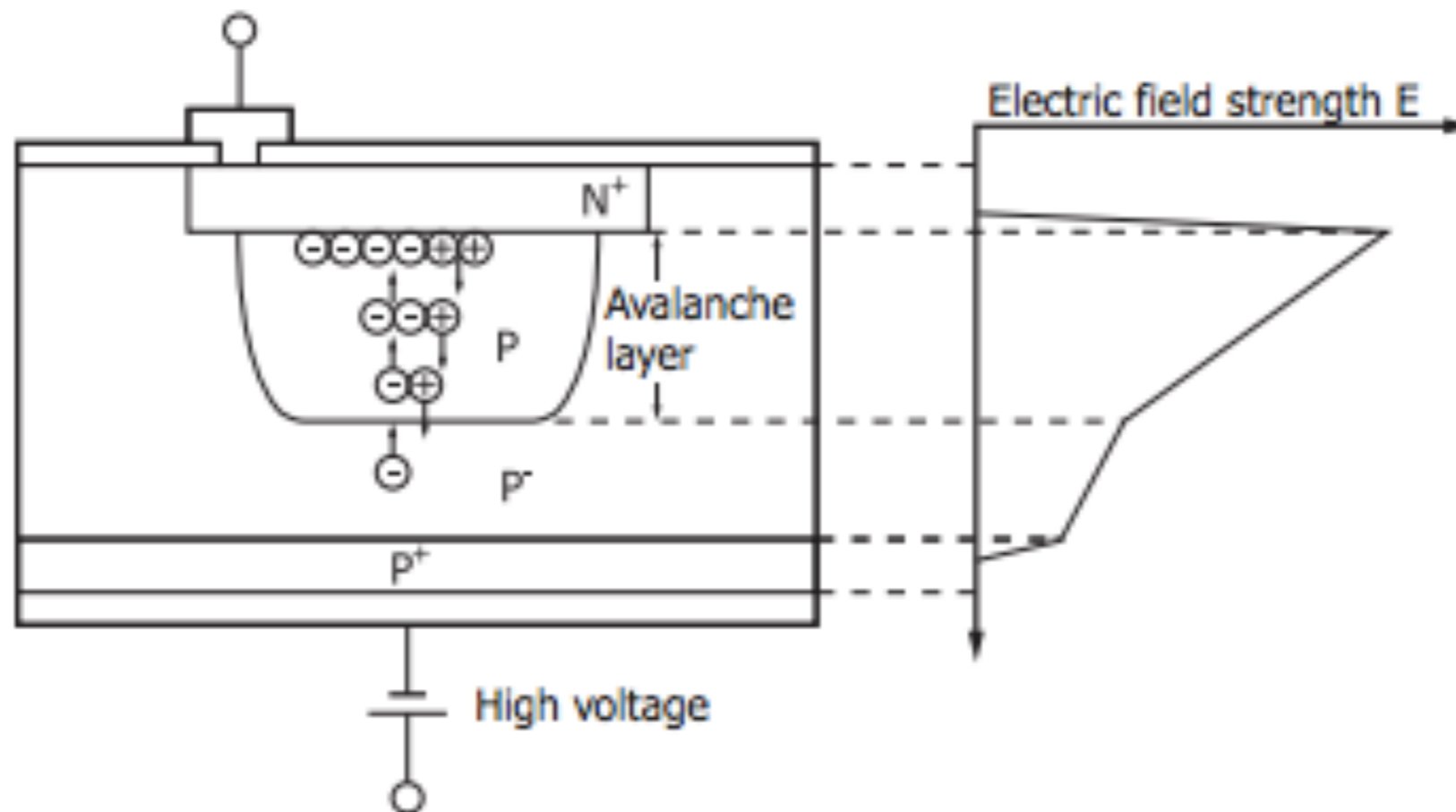


- Avalanche multiplication

# Circuit Design


mppc power supply

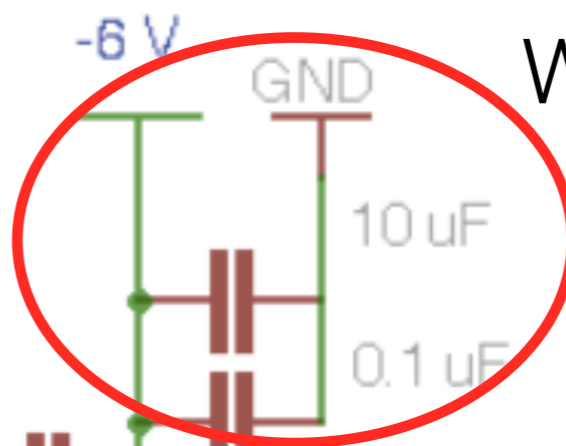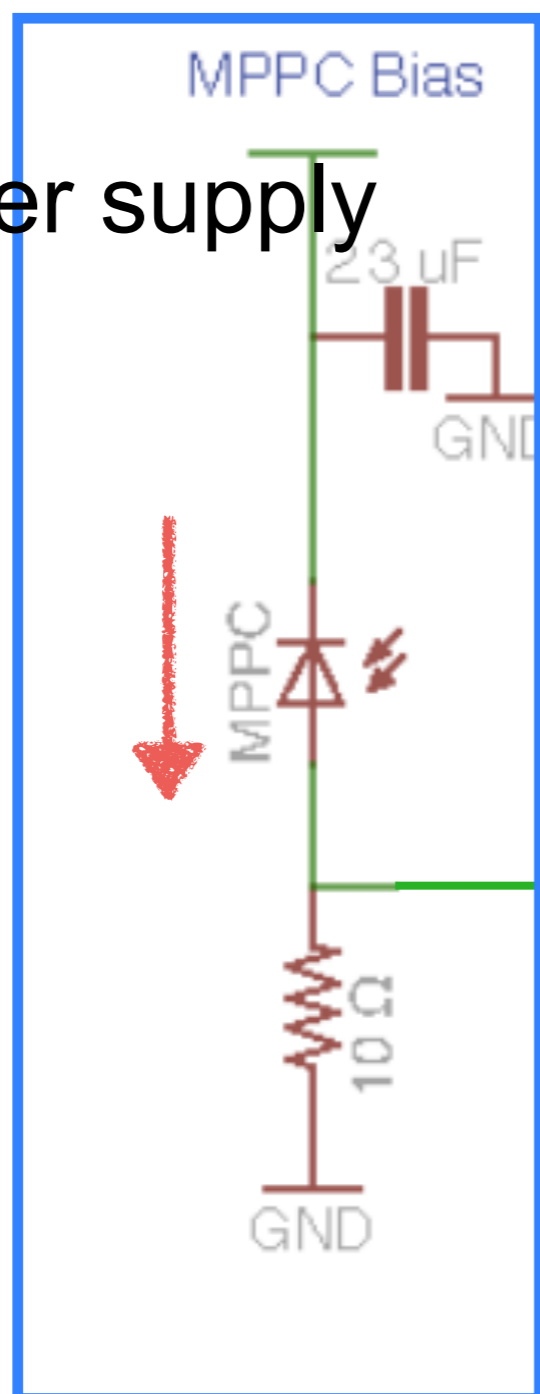


What's going on here?

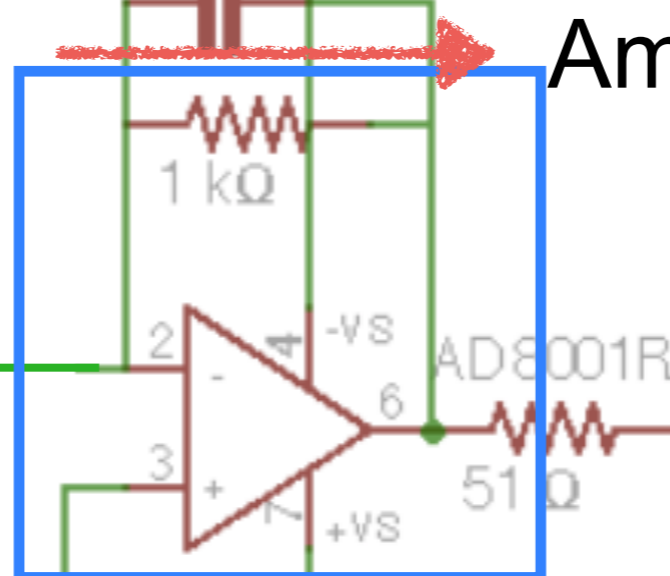




OUTPUT

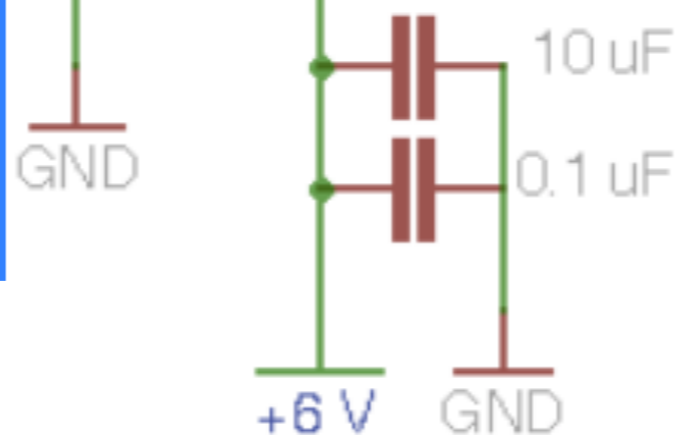

# Bypassing

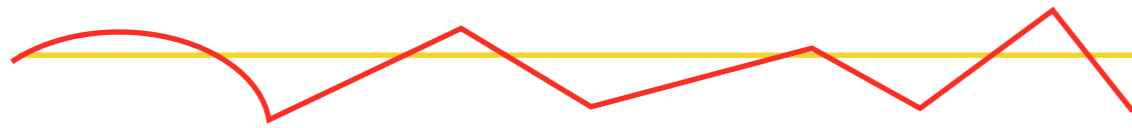

— DC 6 V  
— AC noise

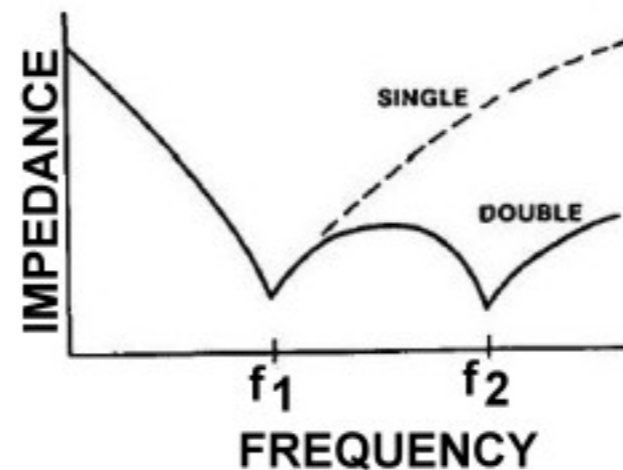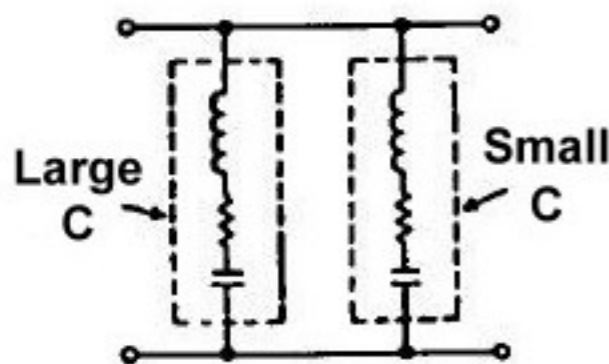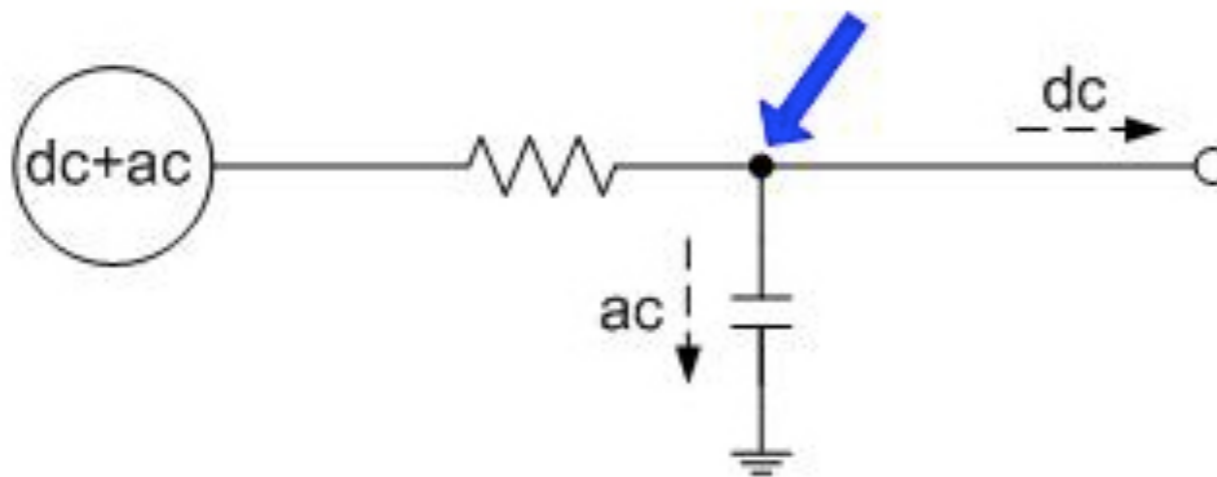


$$X_C = \frac{1}{2\pi fC}$$

Parallel Capacitor Frequency Response



# Negative Feedback Amplifier

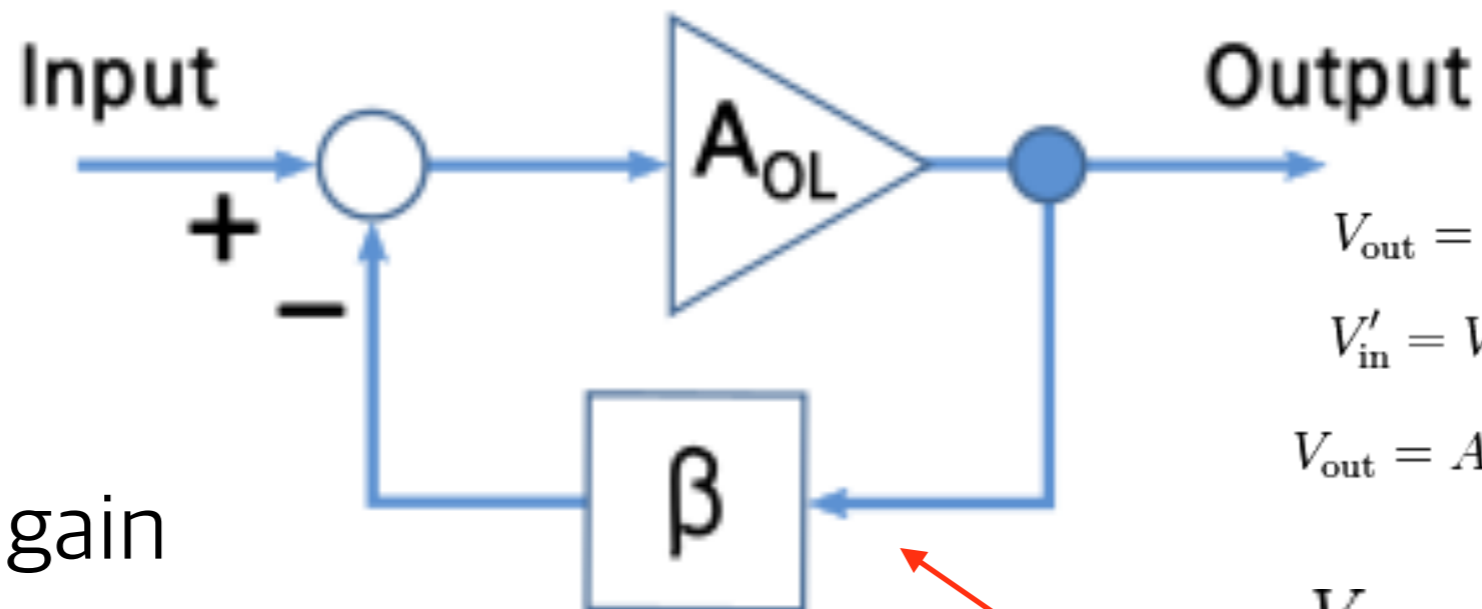


$A_{OL}$ : open loop gain  
 $\beta$ : feedback factor

$$V_{out} = A_{OL} \cdot V'_{in}$$
$$V'_{in} = V_{in} - \beta \cdot V_{out}$$
$$V_{out} = A_{OL}(V_{in} - \beta \cdot V_{out})$$
$$\frac{V_{out}}{V_{in}} = \frac{A_{OL}}{1 + \beta \cdot A_{OL}}$$


Phase upside down

# Transimpedance Amplifier

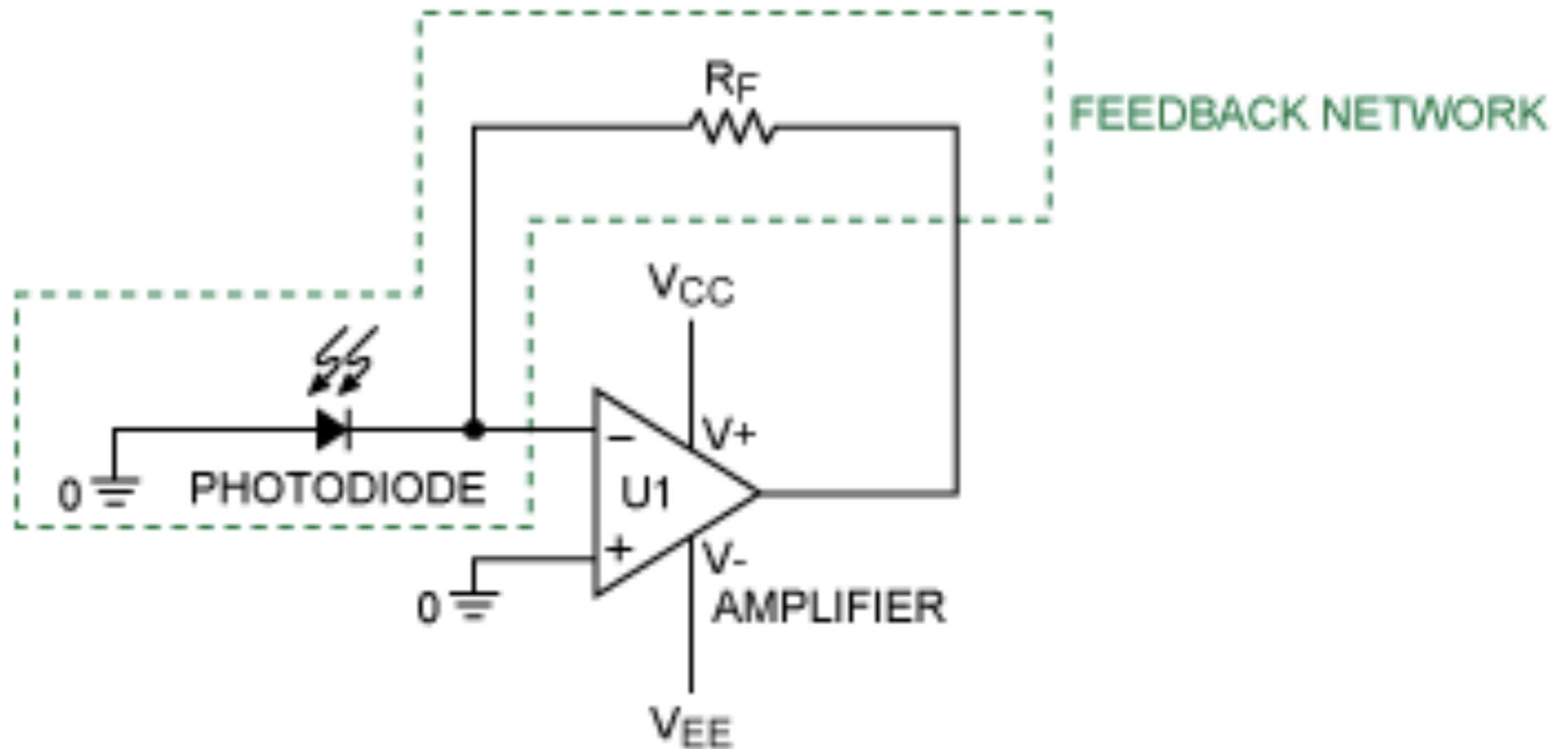





# Equivalent Circuit

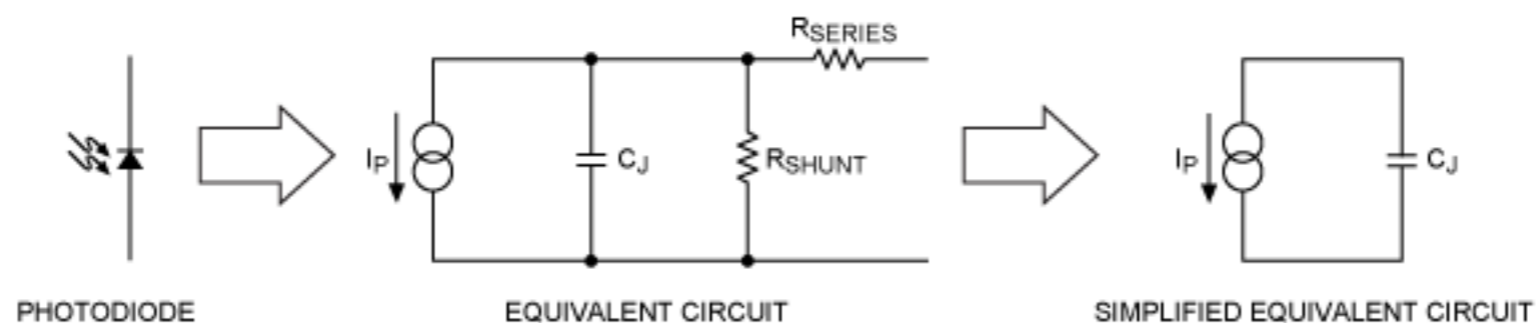

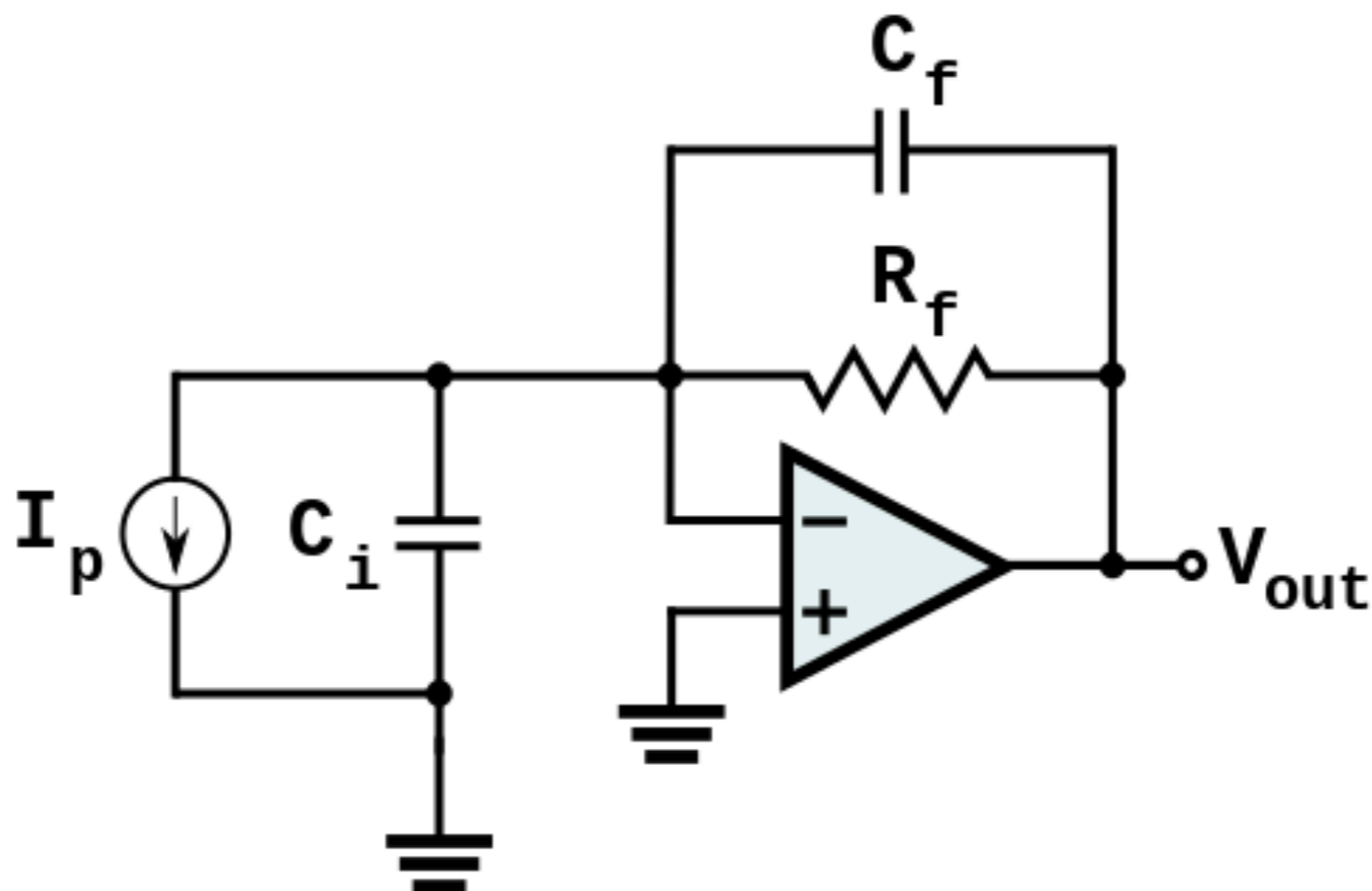$R_{SERIES} = 0$   
 $R_{SHUNT} = \text{Infinity}$



# Feedback Network

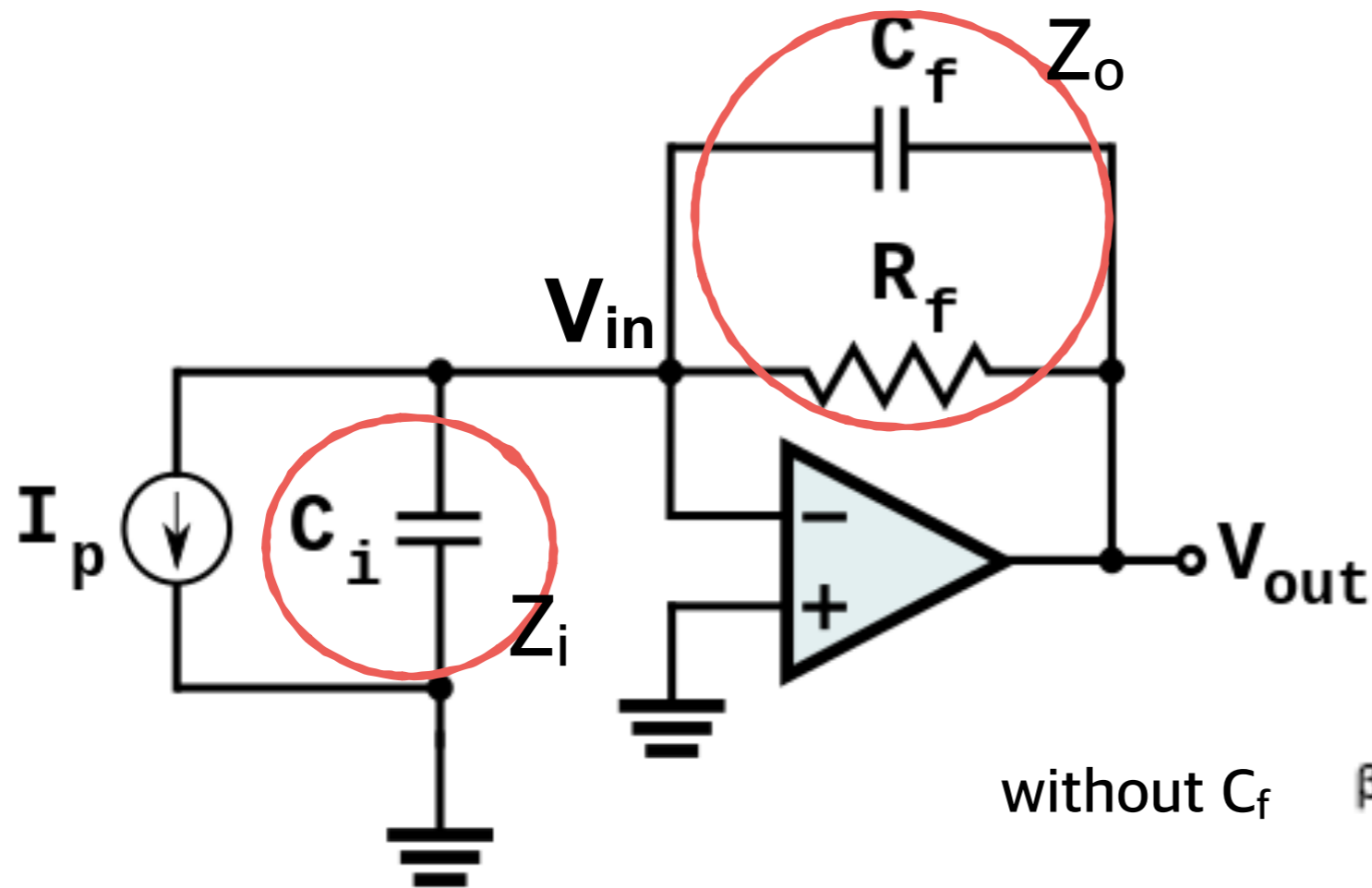

feedback factor  

$$V_{in}/V_{out} = Z_o / (Z_i + Z_o)$$


without  $C_f$

$$\beta(j\omega) = \frac{X_{Ci}}{Z_F + X_{Ci}} = \frac{1}{1 + j\omega R_F C_i}$$

with  $C_f$


$$\beta(j\omega) = \frac{X_{Ci}}{R_F || X_{CF} + X_{Ci}} = \frac{1 + j\omega R_F C_F}{1 + j\omega R_F (C_i + C_F)}$$

# High Frequency Response

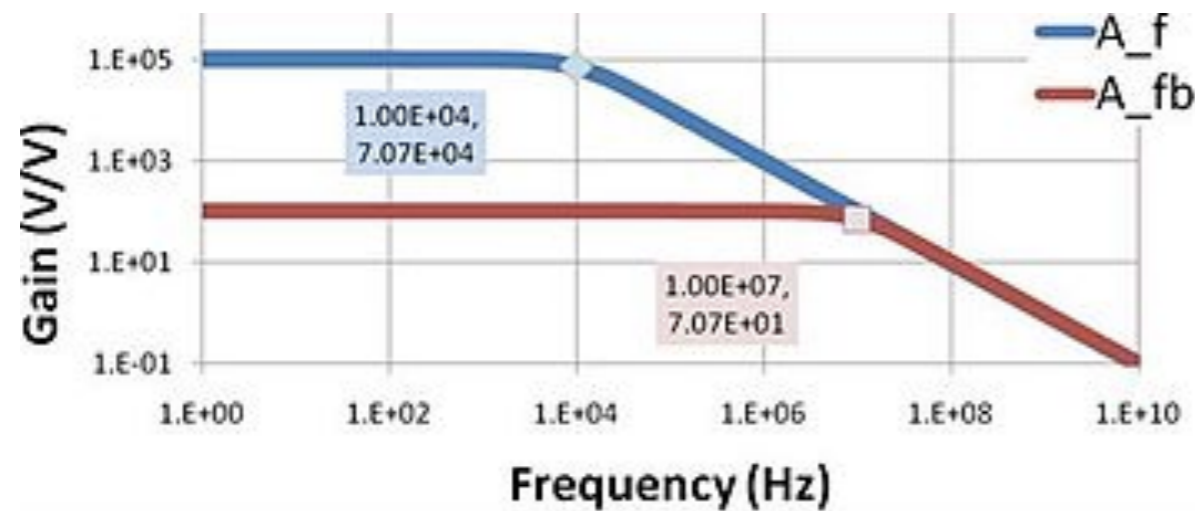


$$A_{OL}(f) = \frac{A_0}{1 + jf/f_c}$$
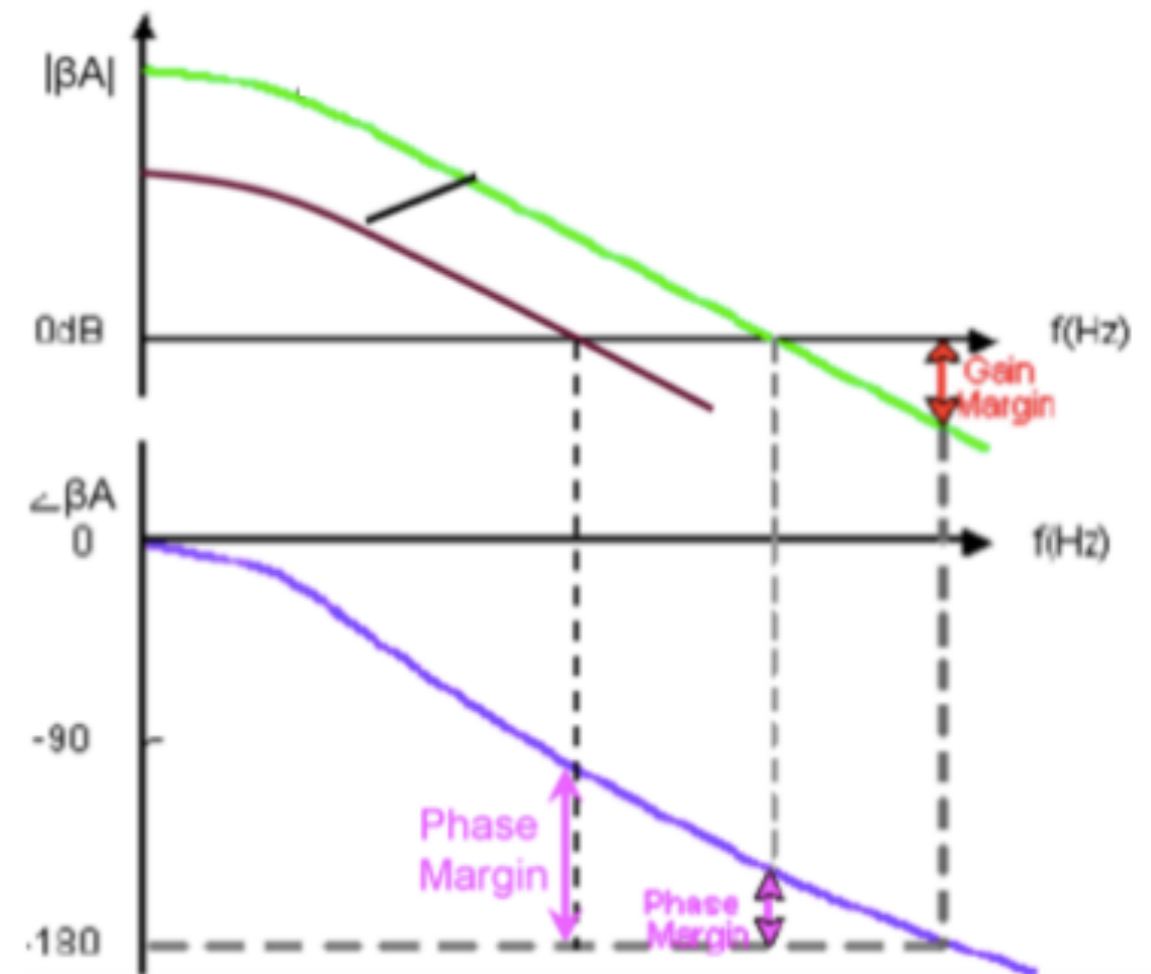
$$\begin{aligned} A_{FB}(f) &= \frac{A_{OL}}{1 + \beta A_{OL}} \\ &= \frac{A_0/(1 + jf/f_c)}{1 + \beta A_0/(1 + jf/f_c)} \\ &= \frac{A_0}{1 + jf/f_c + \beta A_0} \\ &= \frac{A_0}{(1 + \beta A_0) \left(1 + j \frac{f}{(1 + \beta A_0)f_c}\right)} \end{aligned}$$




# LED test

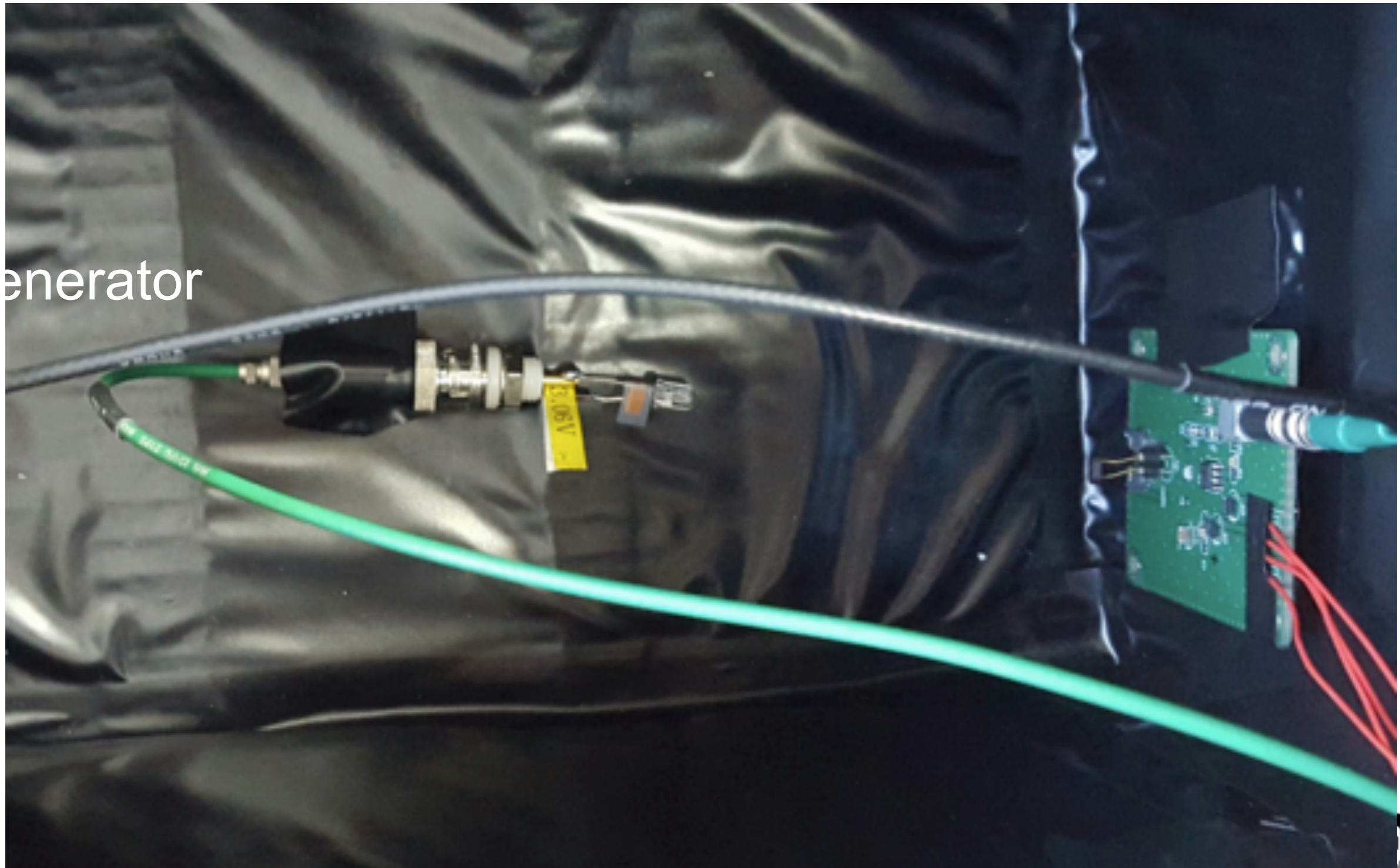




# Results

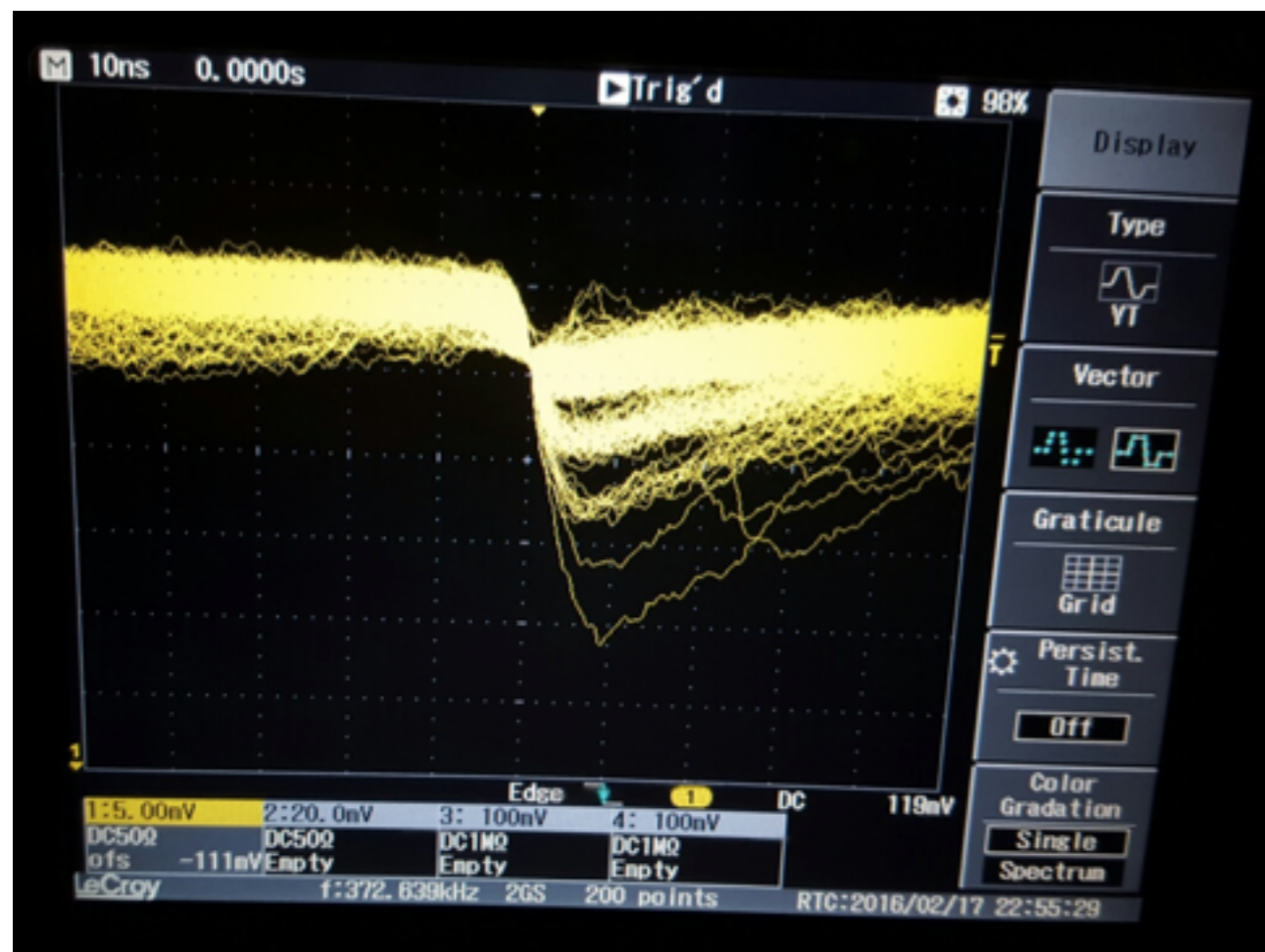


Dark current

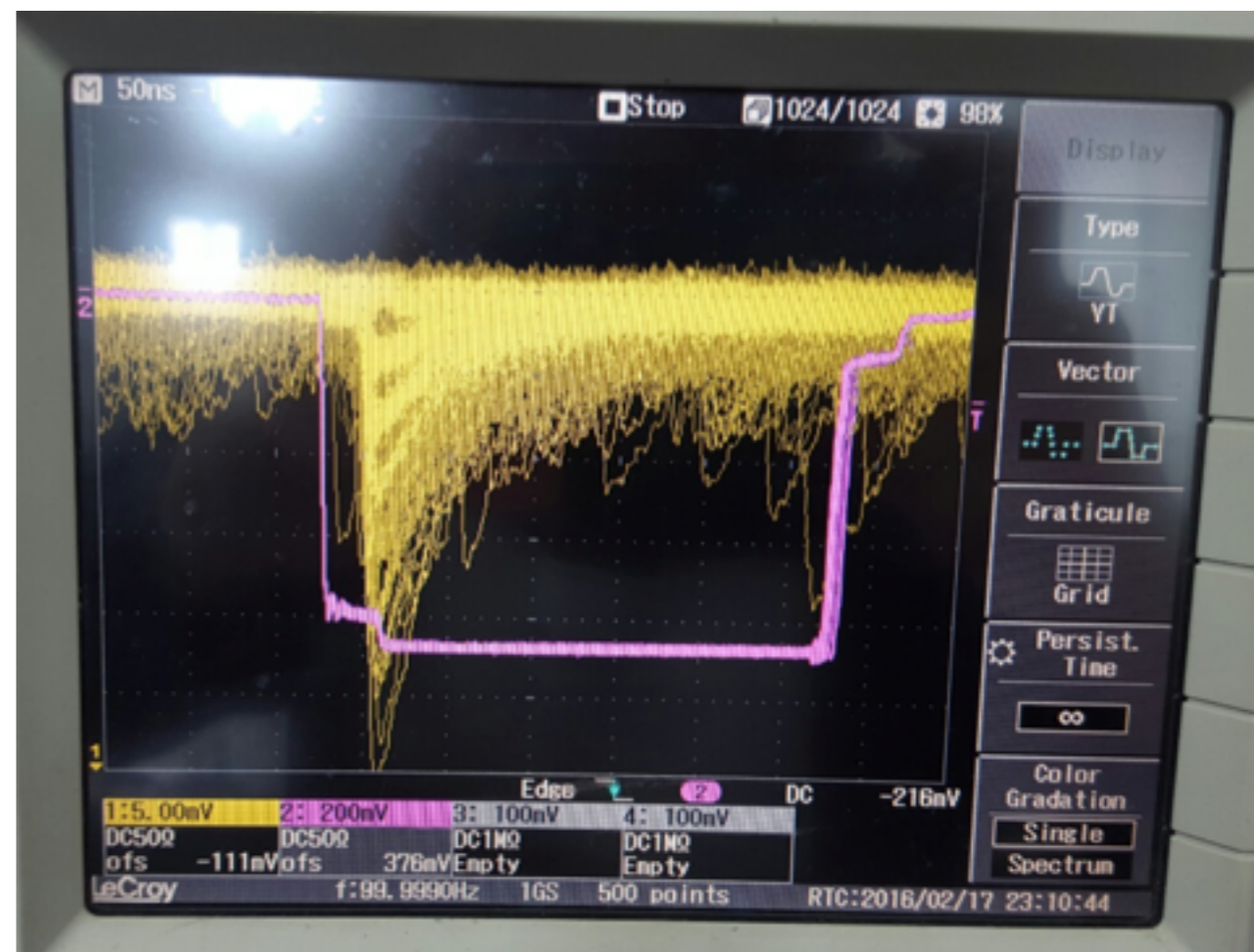


LED signals

# waveform

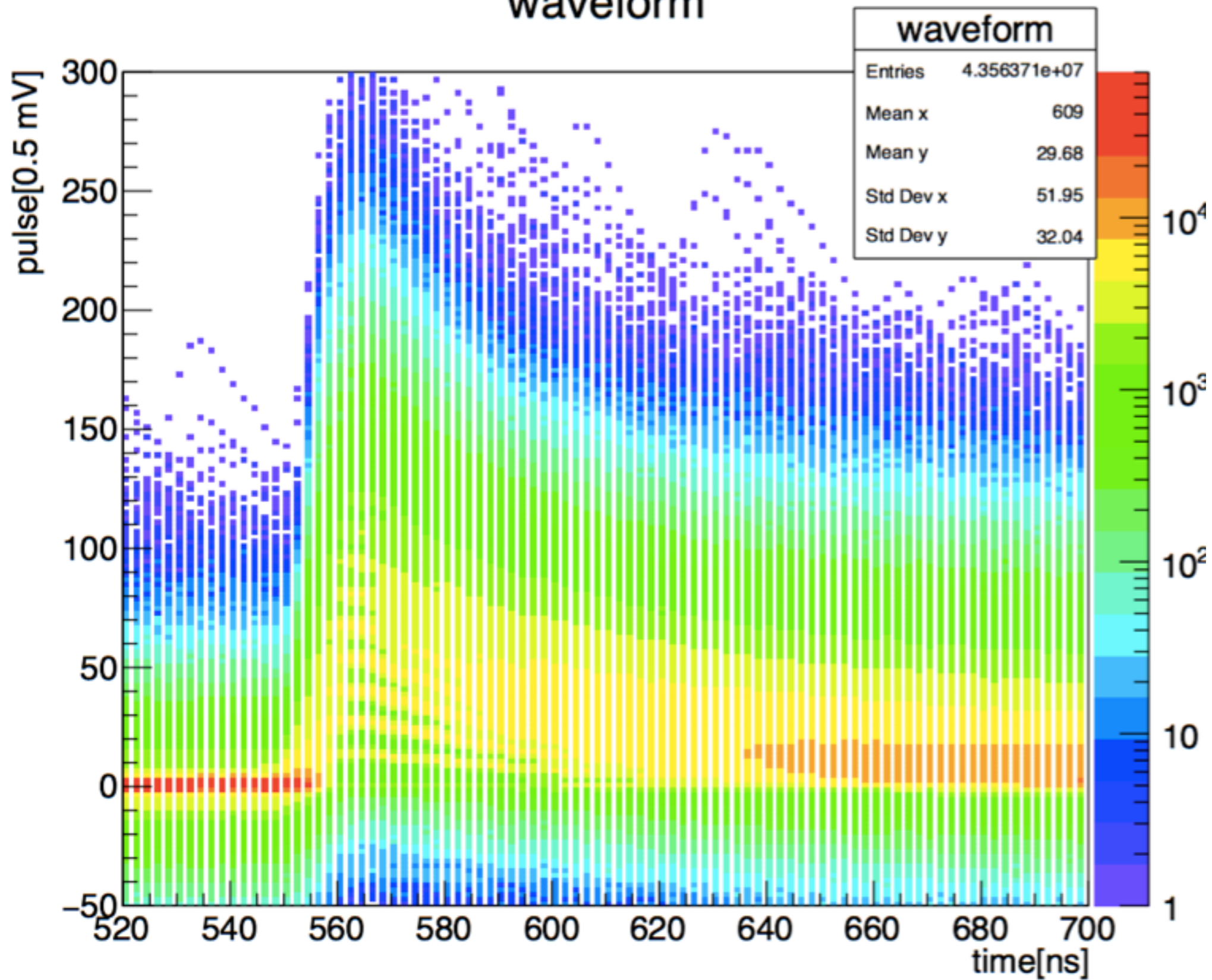

pulse height

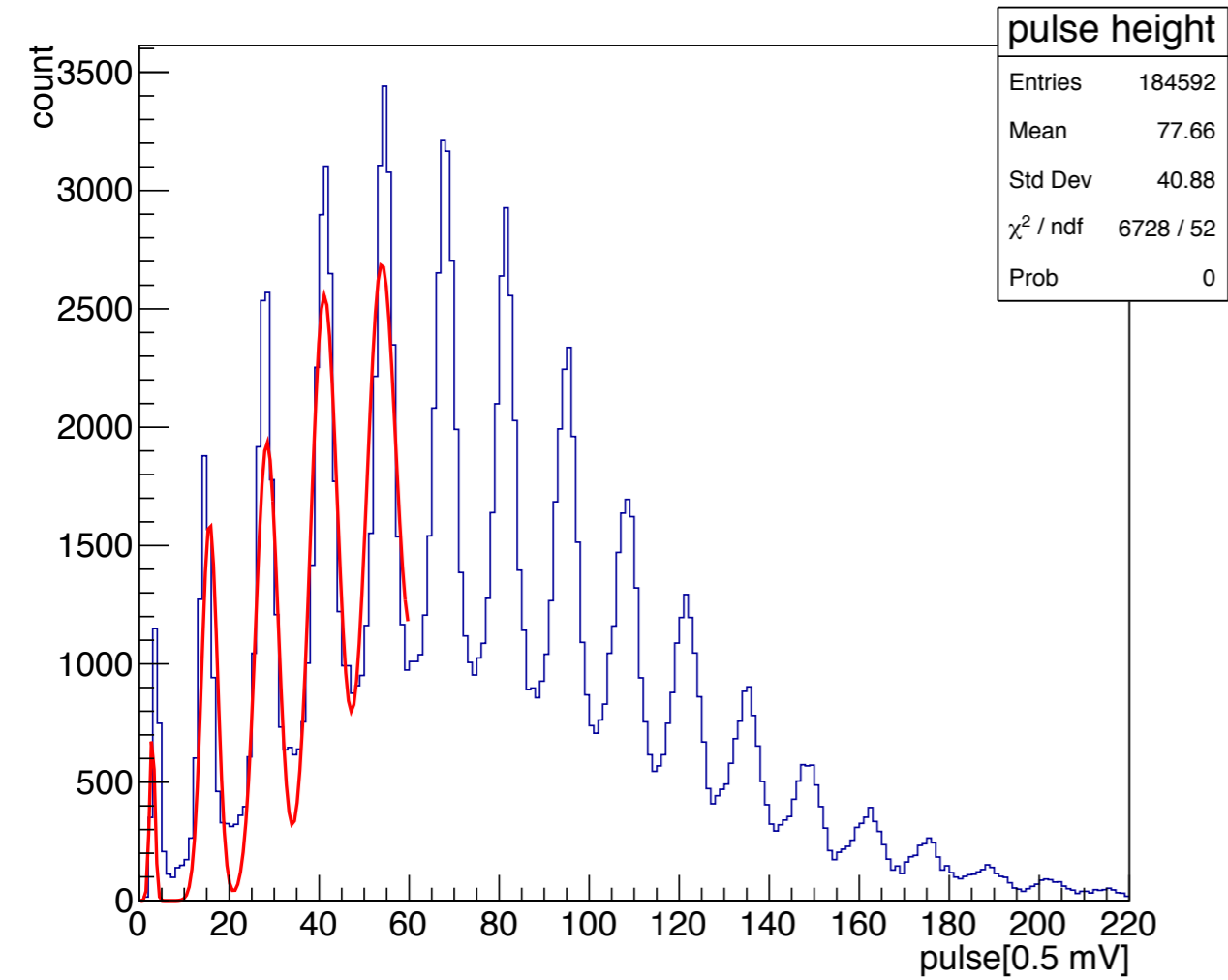

ADC histogram

