

# Equivalent circuit model of MPPC

Korea Univ.  
Wooseung Jung

# GEIGER-APD


$R_S$  : Resistance of the entire APD during a discharge

$R_Q$  : Quenching resistor

$C_J$  : Junction capacitance

typical values

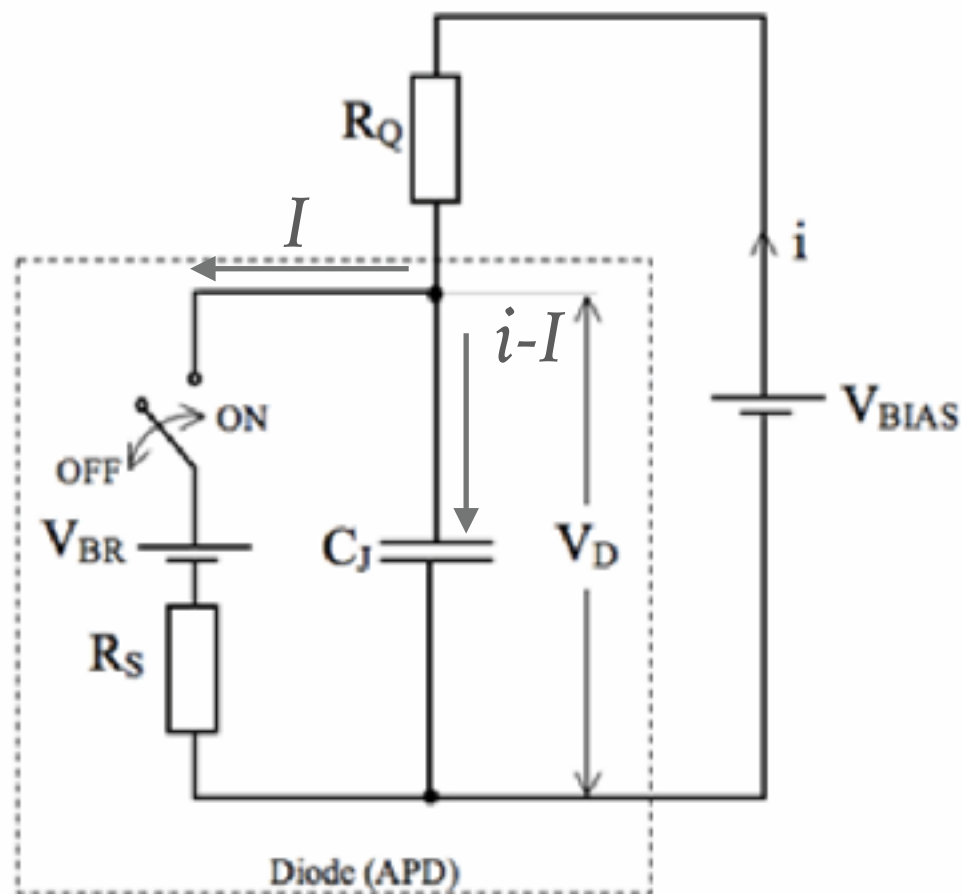$R_S \sim 1 \text{ k}$ ,  $R_Q \sim 150 \text{ k}$ ,  $C_J \sim 0.1 \text{ pf}$



Equivalent circuit of MPPC's single GAPD

By Kirchoff's current law


$$V_{BIAS} - Q/C_j - iR_Q = 0$$

$$V_{BIAS} - V_{BR} - (i - I)R_S - iR_Q = 0$$

$$\tau_r = C_j \frac{(R_S R_Q)}{(R_S + R_Q)} \sim C_j R_S (\because R_Q \gg R_S)$$

$$i = \frac{V_{BIAS} - V_{BR}}{R_S + R_Q} (1 - e^{-t/\tau_r}) \sim \frac{V_{BIAS} - V_{BR}}{R_Q} (1 - e^{-t/\tau_r})$$



$$\tau_r = C_j R_Q$$

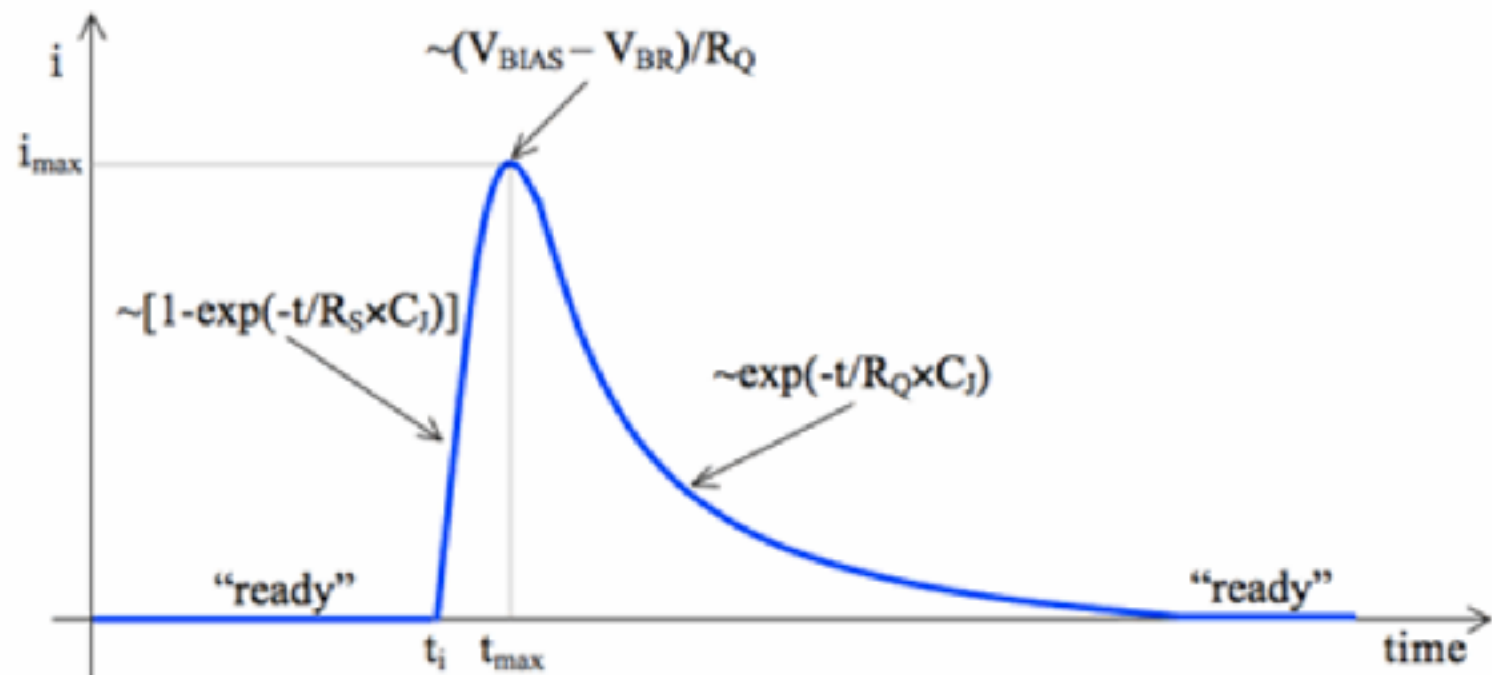

Current flowing through the APD as a function of time


# STRUCTURE OF THE MPPC

Structure of the MPPC

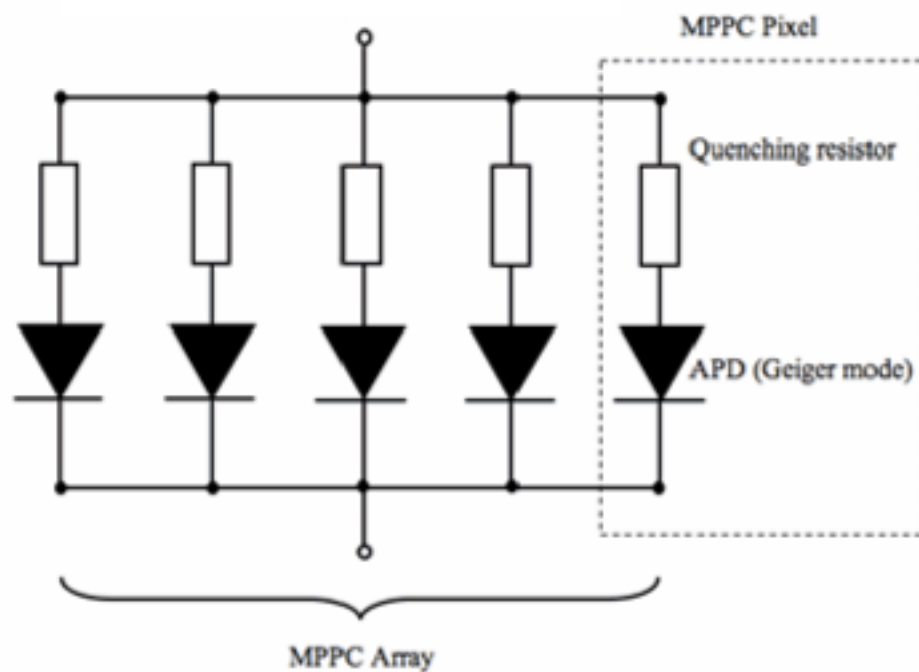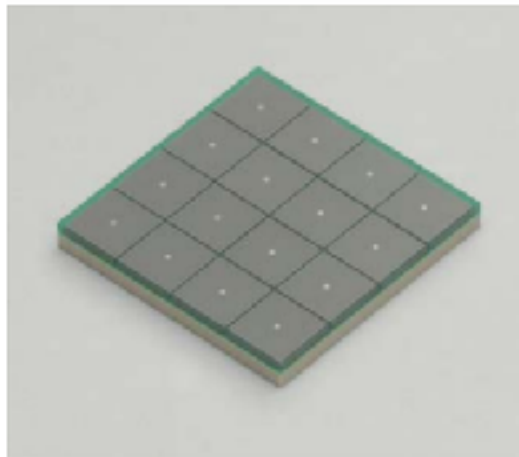

Equivalent circuit of the MPPC

fired pixels(n pixels)

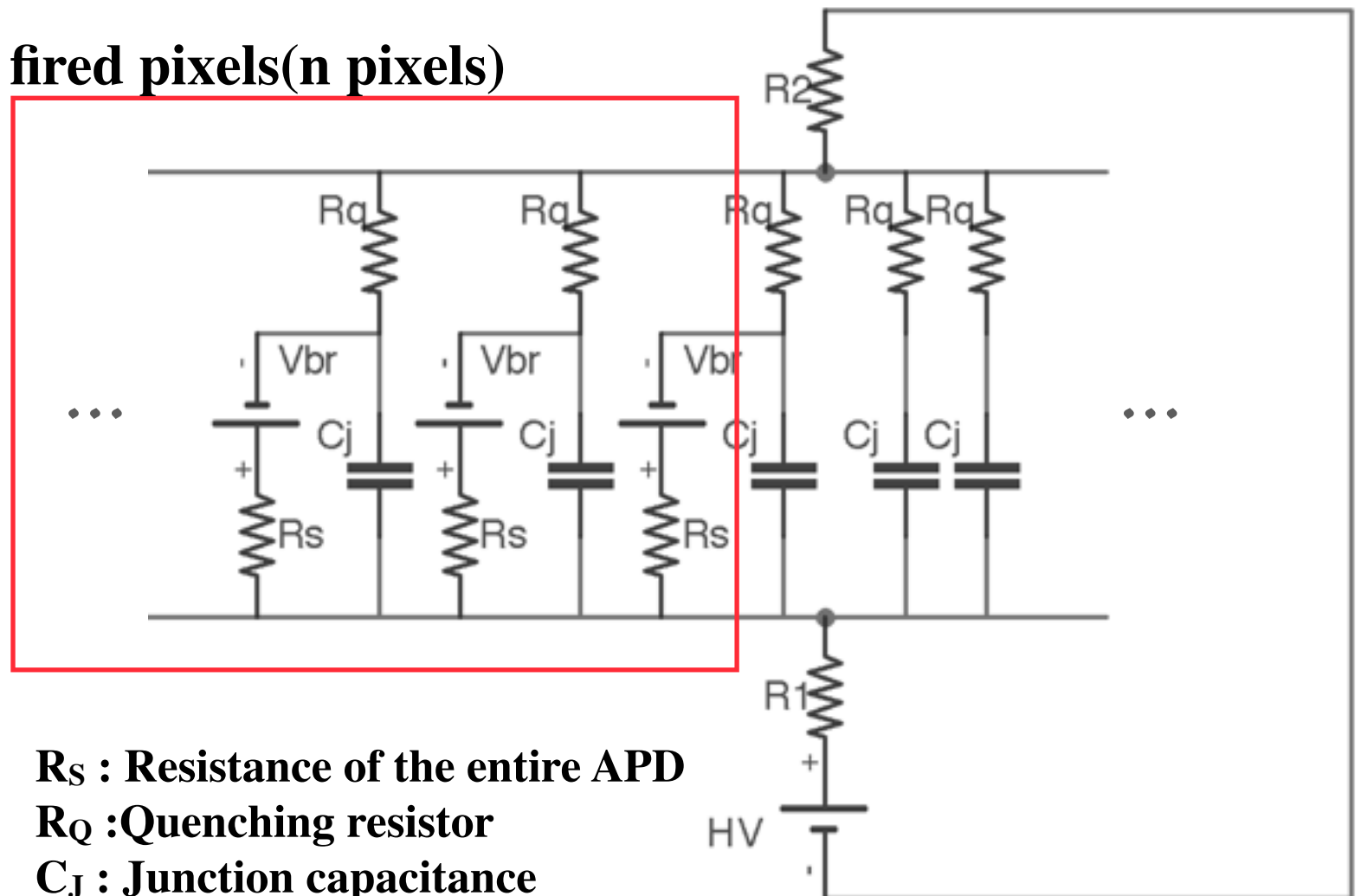


$R_S$  : Resistance of the entire APD  
 $R_Q$  : Quenching resistor  
 $C_J$  : Junction capacitance

# EQUIVALENT CIRCUIT OF THE MPPC

Equivalent circuit of the MPPC



**N:** total # of pixels of the MPPC  
**n:** # of fired pixels of the MPPC

fired pixels(n pixels)

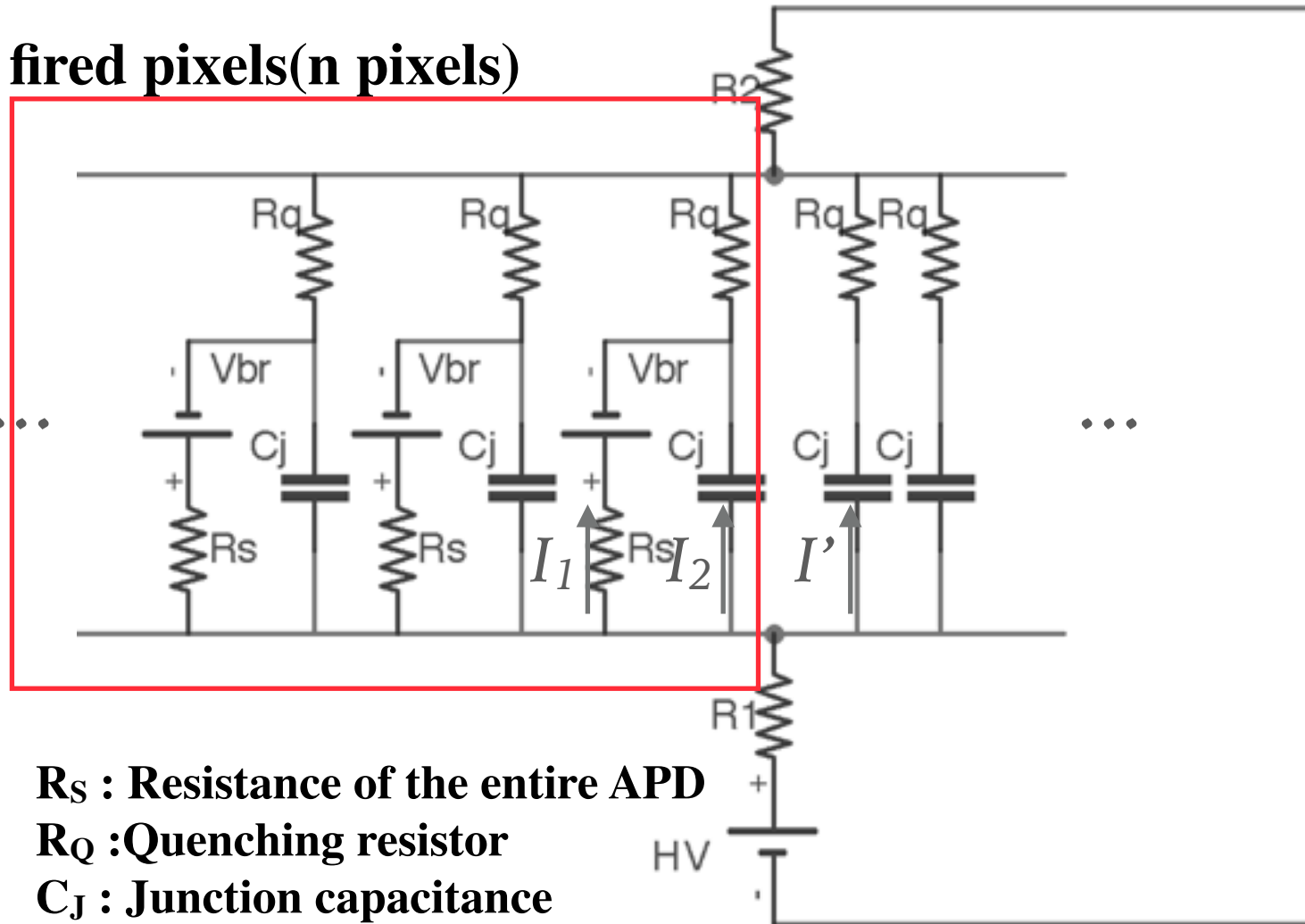


**$R_S$**  : Resistance of the entire APD  
 **$R_Q$**  : Quenching resistor  
 **$C_J$**  : Junction capacitance

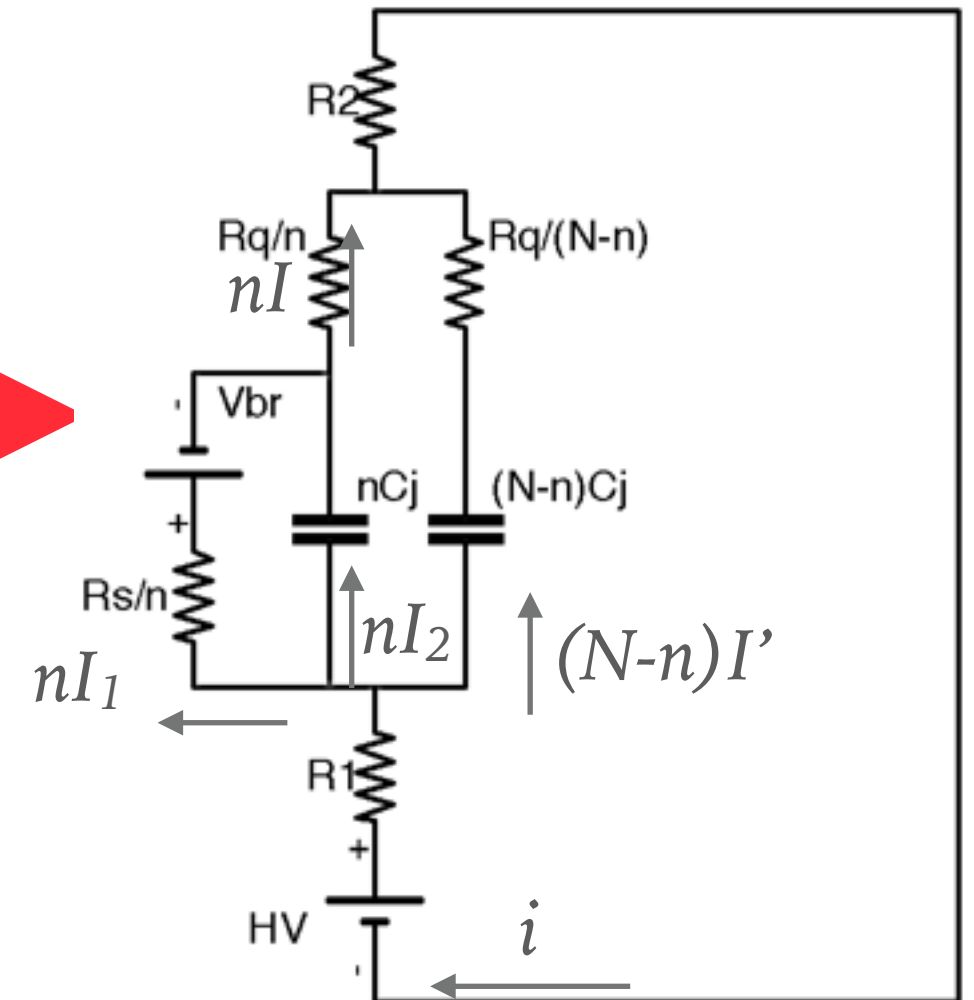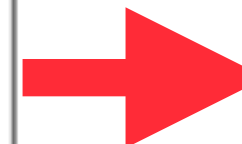**$R_1$  and  $R_2$**  : series resistors in circuit (Let  $R = R_1 + R_2$ )



# EQUIVALENT CIRCUIT OF THE MPPC

## Equivalent circuit of MPPC

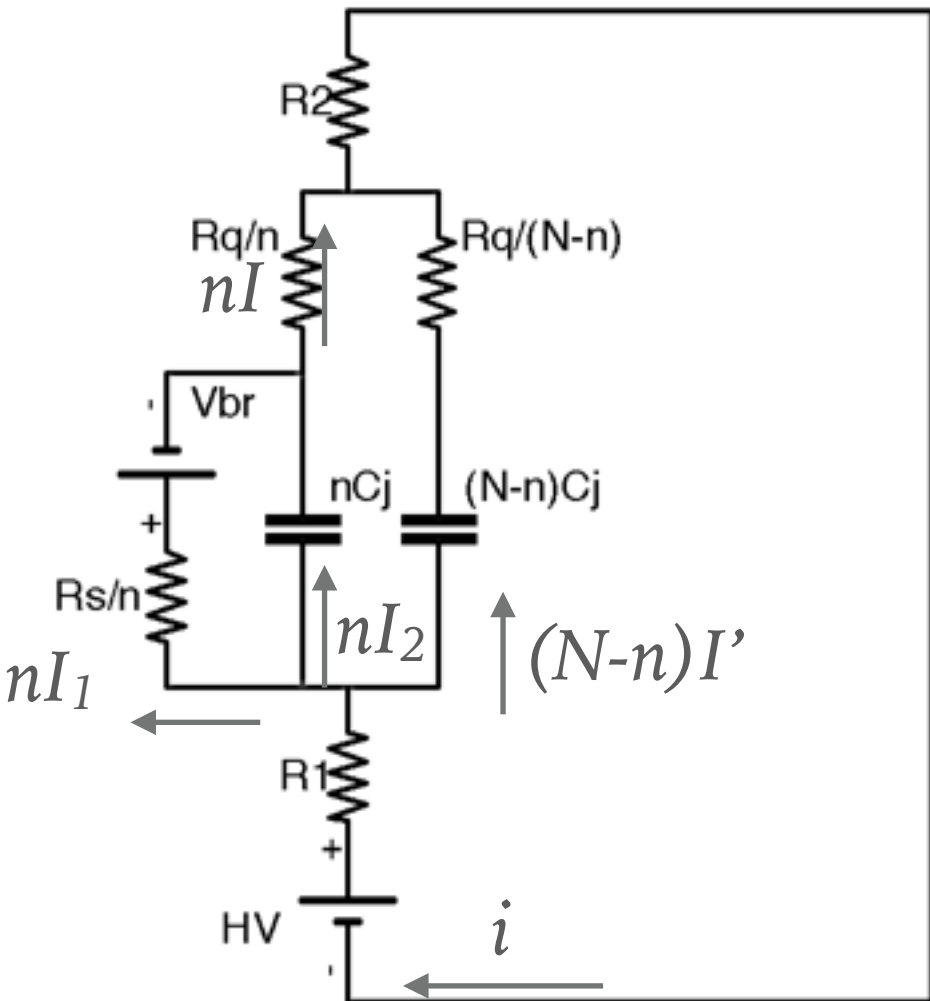

By Kirchhof's current law

$$i = nI + (N-n)I', \quad I = I_1 + I_2$$

$$V_{BIAS} - V_{BR} - iR - I_1 R_S - I R_Q = 0$$

$$V_{BIAS} - iR - Q/C_j - I R_Q = 0$$

$$V_{BIAS} - iR - Q'/C_j - I' R_Q = 0$$

Leading edge

$$\tau_r = C_j R_S$$

$$i = \frac{n(V_{BIAS} - V_{BR})}{nR + R_S + R_Q} (1 - e^{-t/\tau_r}) \sim \frac{n(V_{BIAS} - V_{BR})}{R_Q} (1 - e^{-t/\tau_r})$$

$$I = \frac{n(V_{BIAS} - V_{BR})}{nR + R_S + R_Q} \sim \frac{n(V_{BIAS} - V_{BR})}{R_Q}$$

Trailing edge

$$\tau_t = C_j (R_Q + NR)$$

$R_S$  : Resistance of the entire APD

$R_Q$  : Quenching resistor

$C_J$  : Junction capacitance




$N$ : total # of pixels,  $n$ : # of fired pixels

$R_1$  and  $R_2$  : series resistors in circuit (Let  $R = R_1 + R_2$ )

# PREVIOUS TEST CONDITION

---


MPPC has 16 channels

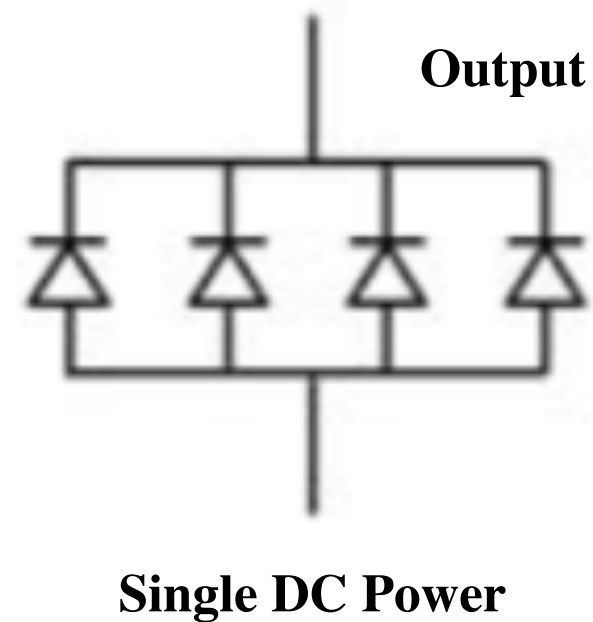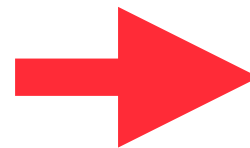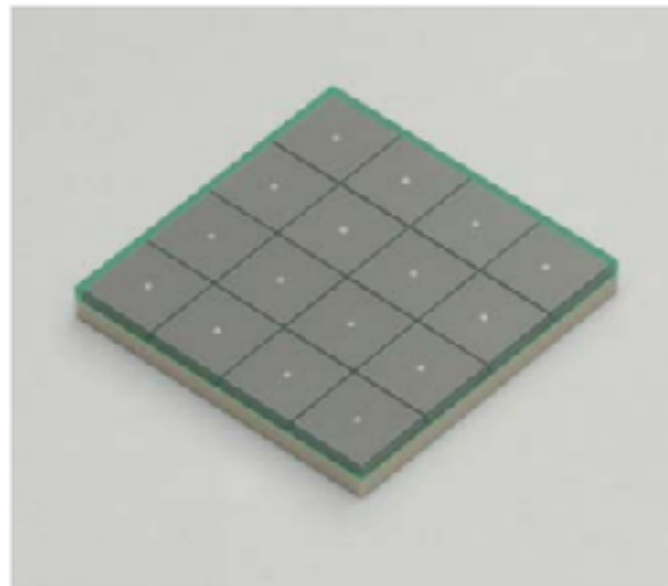

- Sixteen Channels were connected in parallel
- Single DC power applied same voltages for all channels
- Current outputs of every channel's were gathered

# MPPCS IN PARALLEL CONNECTION

Equivalent circuit

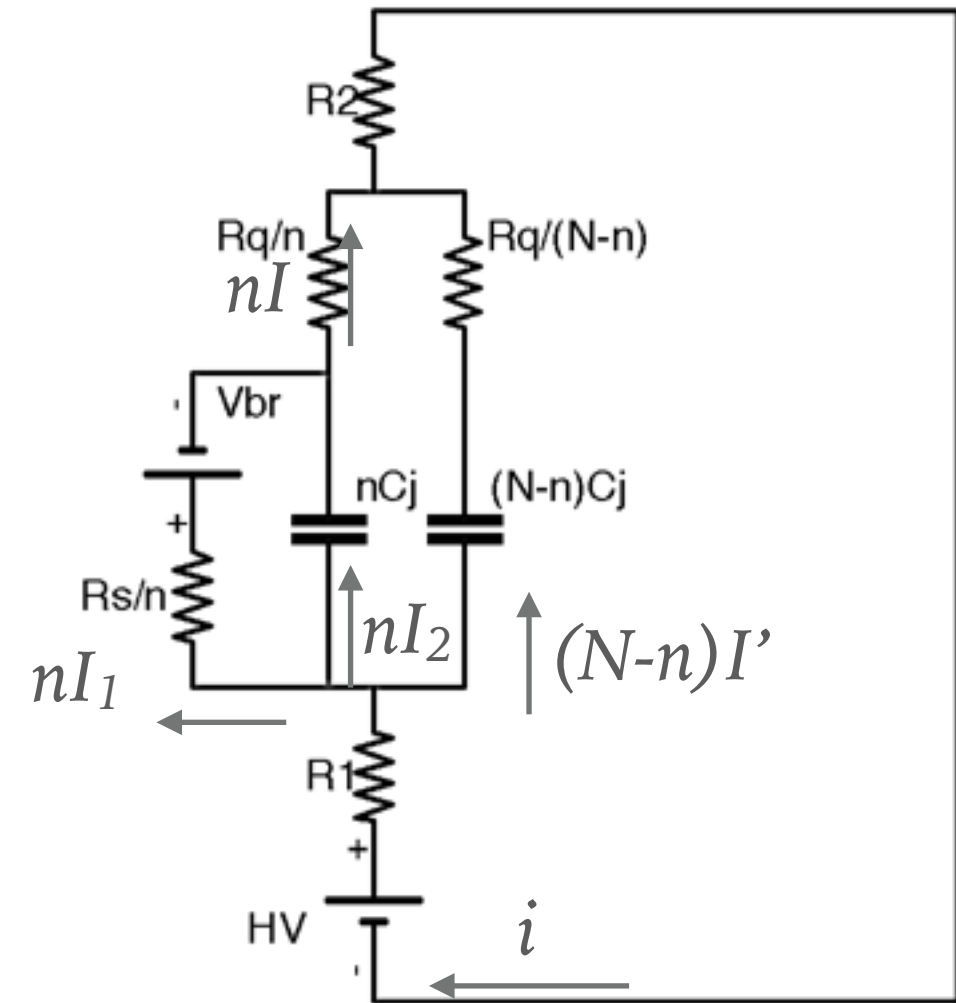

Assume that number of 'a' MPPCs are connected in parallel  
Only one thing is different from single MPPC,  $N \rightarrow aN$

For the leading edge, all parameters and values still remain same

Leading edge

$$\tau_r = C_j R_S$$

$$i = \frac{n(V_{BIAS} - V_{BR})}{nR + R_S + R_Q} (1 - e^{-t/\tau_r}) \sim \frac{n(V_{BIAS} - V_{BR})}{R_Q} (1 - e^{-t/\tau_r})$$

$$I = \frac{n(V_{BIAS} - V_{BR})}{nR + R_S + R_Q} \sim \frac{n(V_{BIAS} - V_{BR})}{R_Q}$$

Time constant of fall time has a term promotional to 'a'  
So, tailing edge become longer

$$\tau_t = C_j R_Q + \underline{a \times C_j N R}$$

$R_S$  : Resistance of the entire APD

$R_Q$  : Quenching resistor

$C_J$  : Junction capacitance

$N$ : total # of pixels,  $n$ : # of fired pixels

$R_1$  and  $R_2$  : series resistors in circuit (Let  $R = R_1 + R_2$ )

# REFERENCE OF MULTI-MPPC BIASING

## MEG Collaboration's test results

Kaneko, D., *Performance of UV-sensitive MPPC for liquid xenon detector in MEG experiment*,

DOI:10.1109/NSSMIC.2013.6829484.



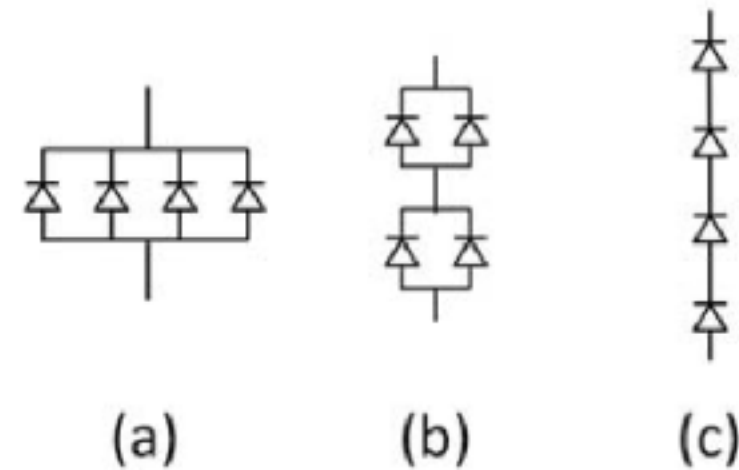


Fig. 10. Connection of 4 MPPCs, 4-parallel, 2-series 2-parallel and 4-series correspond (a), (b) and (c) respectively.

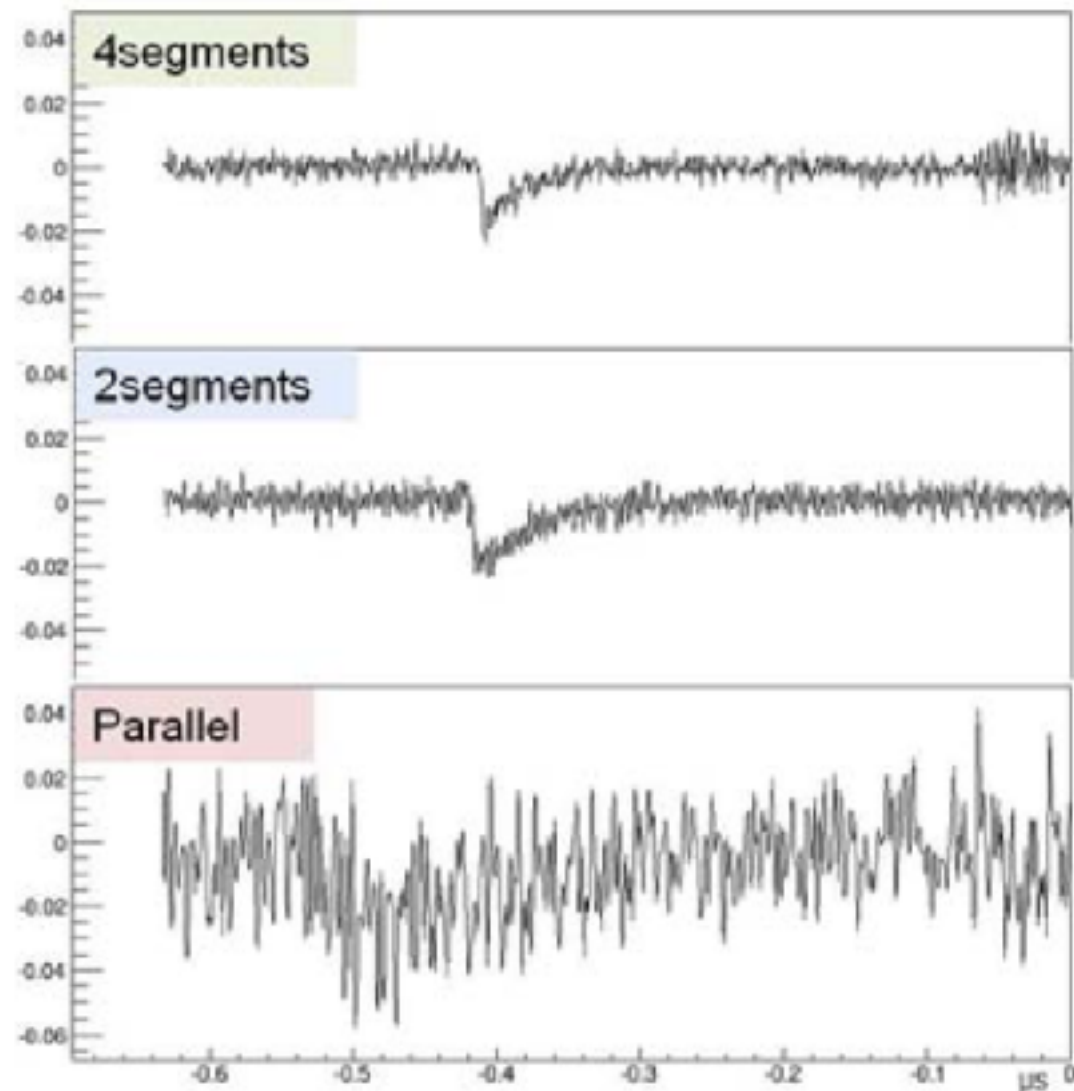

# MPPCS IN SERIES CONNECTION

## Equivalent circuit

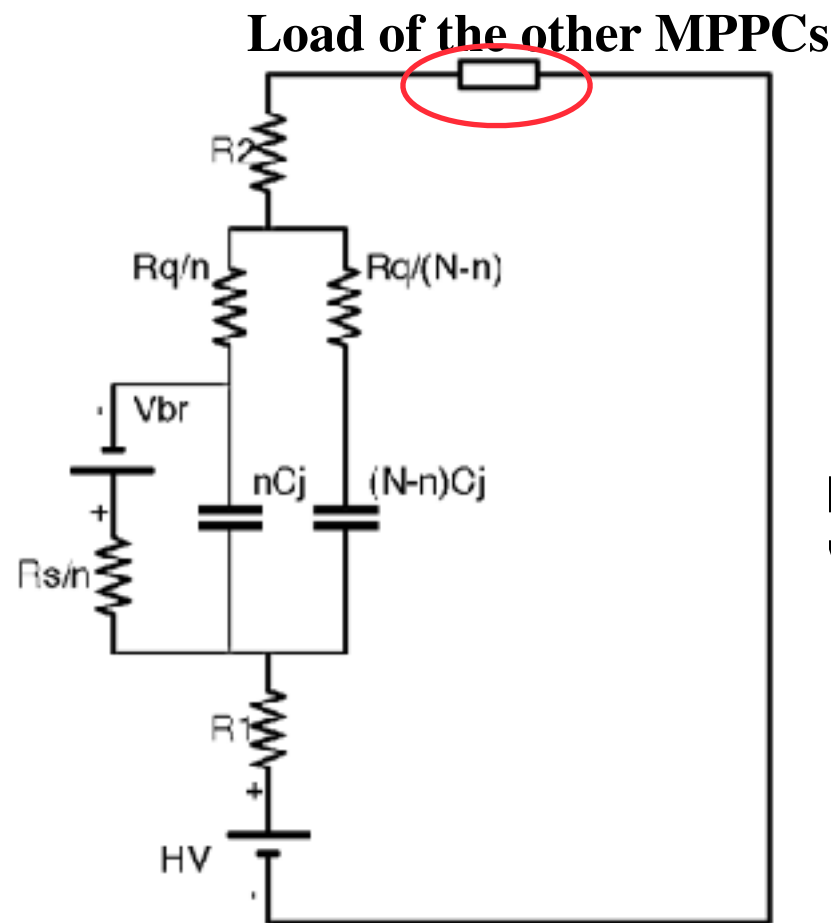

**Bias voltage should become larger in proportional to the number of MPPCs**

Assume the condition that photons are firing only one MPPC (the other cases can be described as a superposition of above situations)

Because of load of additional MPPCs, it is hard to get exact solutions. With another assumption  $dI/dt = 0$ , rising edge shape remains almost same

**But there is a small voltage drop occur through series MPPCs**

$$\tau_T \sim C_j R_S$$

For the tailing edge, time constant become small, So, signal also become shorter

$$\tau_t = C_j R_Q + \underline{C_j N R / a}$$

$R_S$  : Resistance of the entire APD

$R_Q$  : Quenching resistor

$C_J$  : Junction capacitance

$N$ : total # of pixels,  $n$ : # of fired pixels

$R_1$  and  $R_2$  : series resistors in circuit (Let  $R = R_1 + R_2$ )